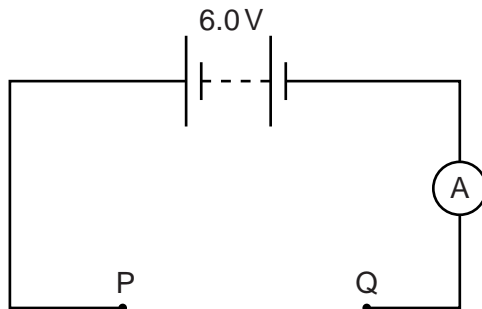


- 1 In the circuit shown in Fig. 9.1, resistors can be connected between terminals P and Q. The e.m.f. of the battery is 6.0V.



**Fig. 9.1**

- (a) Calculate the current shown by the ammeter when a  $12.0\Omega$  resistor and a  $4.0\Omega$  resistor are

- (i) connected in series between P and Q,

current = ..... [2]

- (ii) connected in parallel between P and Q.

current = ..... [3]

- (b) State the relationship between

- (i) the resistance  $R$  and the length  $l$  of a wire of constant cross-sectional area,

.....

- (ii) the resistance  $R$  and the cross-sectional area  $A$  of a wire of constant length.

.....

[2]


(c) The  $12.0\Omega$  and  $4.0\Omega$  resistors in (a) are wires of the same length and are made of the same alloy.

Calculate the ratio:  $\frac{\text{cross-sectional area of } 12.0\Omega \text{ resistor}}{\text{cross-sectional area of } 4.0\Omega \text{ resistor}}$

ratio = ..... [1]

[Total: 8]

2 Fig. 8.1 shows three cells each with e.m.f. 1.5V connected in series.

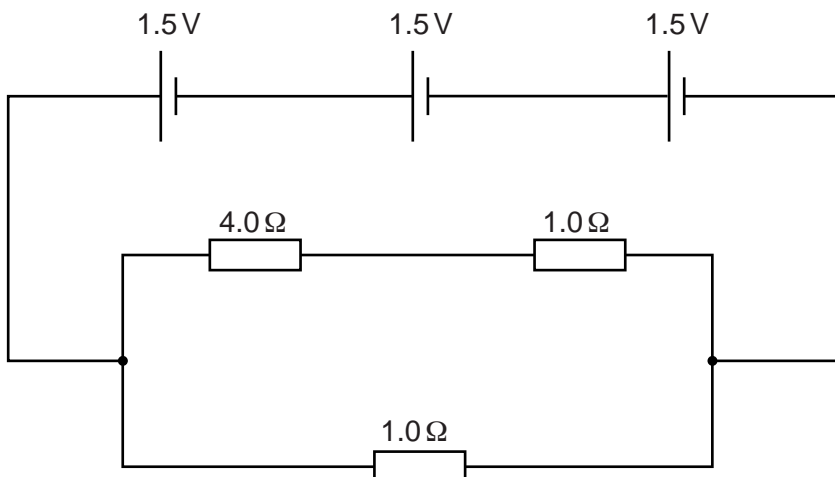

**Fig. 8.1**

(a) Calculate the combined e.m.f. of the cells.

e.m.f. = ..... [1]

(b) Calculate the combined resistance of the three resistors shown in Fig. 8.1.

resistance = ..... [2]

(c) Calculate the current in the 4.0Ω resistor in Fig. 8.1.

current = ..... [3]

(d) Calculate the combined e.m.f. of the cells if one cell is reversed.

e.m.f. = ..... [1]

[Total: 7]

3 (a) Fig. 8.1 shows two resistors X and Y in series.

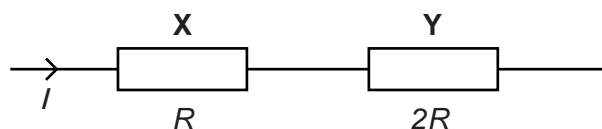


Fig. 8.1

Complete the table below, using only the symbols  $I$  and  $R$ , alone or in combination.

resistor	resistance	current	potential difference	power
X	$R$	$I$		$I^2R$
Y	$2R$		$2IR$	

[3]

(b) Fig. 8.2 represents the system used to transmit electricity from a power station to a factory.

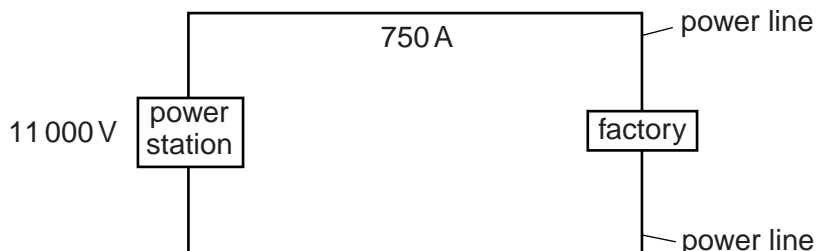


Fig. 8.2

The power station generates 11 000V and supplies a current of 750A. The total resistance of the power lines between the power station and the factory is  $1.5\Omega$ .

Calculate

(i) the power output of the power station,

power = ..... [1]

(ii) the potential difference across the  $1.5\ \Omega$  of the power lines,

potential difference = ..... [1]


(iii) the power supplied to the factory.

power = ..... [3]

[Total: 8]

- 4 A student sets up a circuit containing three identical cells. Each cell has an e.m.f. (electromotive force) of 2.0V.

Fig. 8.1 shows the cells in series with a length of uniform metal wire connected between two terminals K and L, an ammeter and a resistor X.

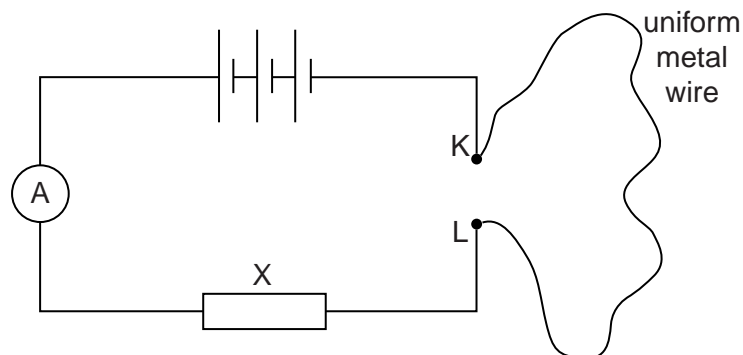

**Fig. 8.1**

- (a) State the total e.m.f. of the three cells in series.

total e.m.f. = ..... [1]

- (b) The ammeter reading is 0.25 A.

- (i) State the name of the unit in which electric charge is measured.

..... [1]

- (ii) Calculate the charge that flows through the circuit in twelve minutes.


charge = ..... [2]

- (iii) The metal wire has a resistance of  $16\ \Omega$ .

Calculate the resistance of resistor X.

resistance = ..... [2]

- (c) The student removes the  $16\Omega$  wire from the circuit and cuts it into two equal lengths. He then connects the two lengths in parallel between K and L, as shown in Fig. 8.2.

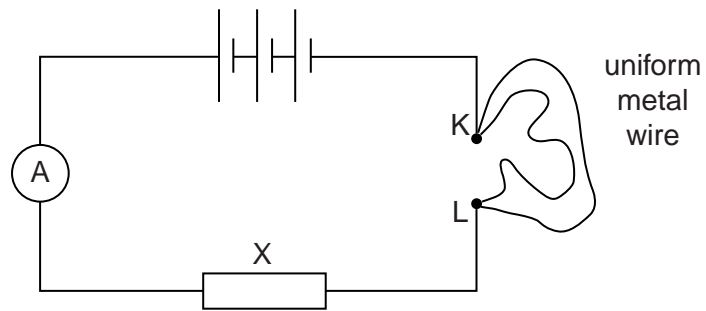

**Fig. 8.2**


Calculate the resistance of the two lengths of wire in parallel.

resistance = ..... [3]

[Total: 9]



5 Fig. 9.1 shows the circuit that operates the two headlights and the two sidelights of a car.

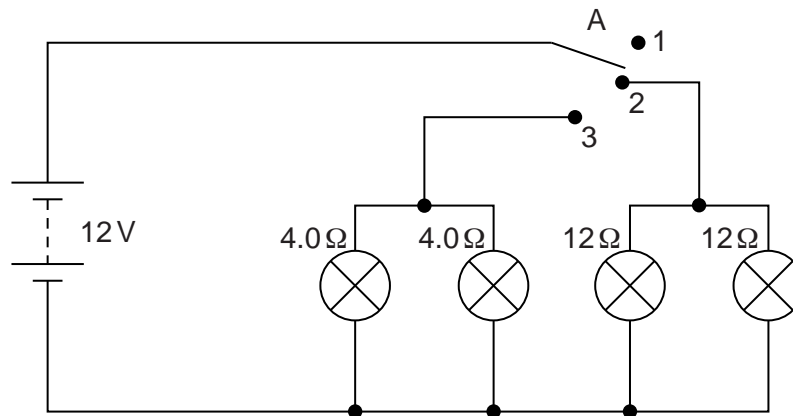

**Fig. 9.1**

Two of the lamps have resistances of  $4.0\Omega$  when lit. The other two lamps have resistances of  $12\Omega$  when lit. Switch A can be connected to positions 1, 2 or 3.

**(a)** State what happens when switch A is connected to

- (i)** position 1, .....
- (ii)** position 2, .....
- (iii)** position 3. ....

[1]

**(b) (i)** State the potential difference across each lamp when lit.

potential difference = ..... [1]

**(ii)** Calculate the current in each  $12\Omega$  lamp when lit.

current = ..... [2]

(c) Show, with reasons for your answer, which type of lamp,  $4.0\Omega$  or  $12\Omega$ , has the higher power.

.....

.....


.....

..... [3]

[Total: 7]

- 6 (a) An electrical safety expert is inspecting a laundry. The main workroom has a very hot and damp atmosphere.

The safety expert recommends that normal domestic light switches, as shown in Fig. 9.1, are replaced.

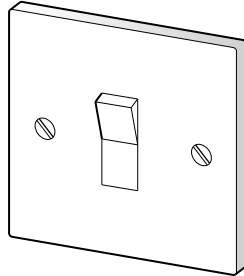

**Fig. 9.1**


- (i) Explain why this recommendation is made.

.....  
.....  
.....  
..... [2]

- (ii) Suggest how the lights should be switched on and off.

.....  
.....  
.....  
..... [1]

(b) Fig. 9.2 shows an aircraft being refuelled through a rubber hose.

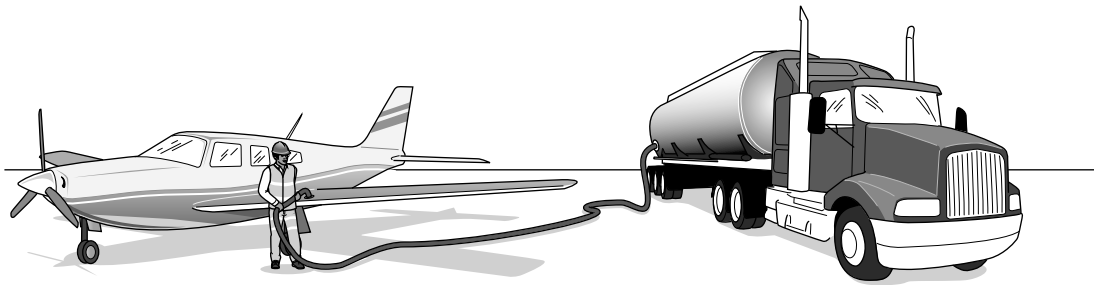

**Fig. 9.2**

(i) Suggest how fuel flowing through the hose can cause a large build-up of electric charge on the aircraft.

.....  
.....  
.....  
..... [2]

(ii) The aircraft is refuelled on a particular day when the tyres and wheels are wet.

Explain why there will be no large build-up of charge in this case.

.....  
.....  
.....  
..... [1]

[Total: 6]