

---

1	A	magnet OR magnetised	F	B1
	B	magnet OR magnetised	F	B1
	C	iron OR unmagnetised	C	B1
	D	aluminium	C	<u>B1</u>
				<u>4</u>

---

2 (a)	$I = V/R$ or $12/8$ $= 1.5 \text{ A}$	1	
		1	
(b) (i)	$10(\Omega)$	1	
	(ii) $2(\Omega)$	1	2
(c)	power = $VI$ or $I^2R$ or $V^2/R$ $= 72\text{W}$	1	
		1	2
(d) (i)	$12(\text{V})$	1	
	(ii) $6(\text{V})$	1	2
(e) (i)	(resistance) less	1	
	(ii) (resistance) less	1	
			(10)

3 (a) (i)	use of charge = $It$ or $I = 90/45$ current = $2 \text{ A}$	C1	
		A1	
(ii)	resistance = voltage/current or $6/2$ resistance is $3 \text{ ohm}$	C1	
		A1	
(iii)	energy = $Vit$ or $Vq$ or $6 \times 90$ energy is $540 \text{ J}$	C1	
		A1	6
(b)	idea of energy transfer is $(6) \text{ J/C}$	C1	
		A1	2
			[8]

4 (a)	current = power/voltage or $150/12$ value is 12.5 A	C1 A1	2
(b) (i)	sum of currents at junction = current after junction/ $12.5 \text{ A} = 5.0 \text{ A} + I$ value is 7.5 A	C1 A1	
(ii)	power = $VI$ or is $7.5 \times 12$ e.c.f from (i) value is 90 W	C1 A1	
(iii)	resistance = voltage/current or $12/7.5$ e.c.f. from (i) but not from (a) value is $1.6\Omega$	C1 A1	6
			[8]

5	a(i) steel	1	A1	
	(ii) insert bar in coil (switch on, leave, switch off)	1	B1	
	(iii) to control/measure current or stop circuit/coil overheating	1	B1	3
	b(i) $R = 12/4$ $= 3 \text{ ohms}^*$	2	A1	
	(ii) $P = 12 \times 4$ $= 48 \text{ W}^*$	2	A1	
	(iii) $E = 48 \times 5$ $= 240 \text{ J}^*$	2	A1	6
	c(i) 5 (V)	1	A1	
	(ii) sum of p.d.'s = circuit supply p.d. above + detail eg across each component/ in closed circuit etc	2	A1	3
				QT 12